

RAQ Issue 178: Wide Voltage Range Automotive Circuit Protector

Albert Hinckley, Product Evaluation Engineer

Question:

Are there overvoltage and undervoltage protection devices available, especially for automotive applications?



Answer:

There are specific power path controllers available to protect your system.

Introduction

Ignition cranking during startup and load dumps during shutdown are common sources of voltage transients on an automotive supply line. These undervoltage (UV) and overvoltage (OV) transients can have significant magnitudes and will damage circuits that are not designed to operate during these extremes. Specialized UV and OV protection devices have been developed to disconnect sensitive electronics from power supply transients.

The [LTC4368](#) is an example of a specialized UV and OV protection device. It utilizes a window comparator to monitor and validate the input supply. The supply voltage is monitored by a resistive divider network connected to the UV and OV monitor pins. The window comparator output drives the gates of two N-channel MOSFETs that make or break the connection between the supply and the load.

The LTC4368's window comparator is designed with 25 mV of hysteresis on its monitor pins to improve noise immunity. Hysteresis can prevent false MOSFET on/off switching due to ripple or other high frequency oscillations on the supply line. The 25 mV of hysteresis in the LTC4368 is equivalent to 5% of the monitor pin thresholds and is common for UV and OV protection devices.

For their own protection or to reduce ignition loading, some automotive accessory circuits must be disconnected from the supply line during startup or shutdown. Due to the large transients involved, these circuits may require more hysteresis than the LTC4368 can provide alone. For such applications, the increased hysteresis requirement can be satisfied by matching the LTC4368 with a supply monitor that has adjustable hysteresis, such as the [LTC2966](#). Figure 1 is an example of a wide voltage range automotive circuit protector. In this circuit, the LTC2966 assumes the role of the window comparator and the LTC4368 is responsible for connecting the load to the supply.

Automotive UV/OV and Overcurrent Monitor with Circuit Protection

The solution shown in Figure 1 protects electronics that are sensitive to undervoltage, overvoltage, and overcurrent transients present on an automotive supply.

The LTC2966 monitors reverse voltage, undervoltage, and overvoltage conditions. Monitoring thresholds and hysteresis levels are configured by the resistor networks on the INH and INL pins and the voltages on the RS1 and RS2 pins. OUTA is the UV window comparator output and OUTB is the OV window comparator output. The polarity of these outputs can be selected to be inverting or noninverting with respect to the inputs via the PSA and PSB pins. In Figure 1, they are configured to be noninverting. The OUTA and OUTB outputs from the LTC2966 are pulled up to the REF pin of the LTC2966 and are fed directly to the UV and OV pins of the LTC4368.

The LTC4368 provides reverse current and overcurrent protection. The size of the current sense resistor, R11, determines the reverse current and overcurrent levels. The LTC4368 decides if the load should be connected to the supply based on its overcurrent comparators as well as the monitoring information from the LTC2966. The UV, OV, and SENSE (overcurrent) pins all participate in the decision-making process. If conditions are satisfied for all three pins, then the GATE pin pulls above V_{OUT} and the load will connect to the supply through the dual N-channel MOSFET power path. If any of the three pins become dissatisfied, the GATE pin pulls below V_{OUT} and the load is disconnected from the supply.

Automotive applications that are powered directly from the battery are subjected to large voltage swings during engine start and stop. In this protection solution, voltage monitoring thresholds are based on nominal operating voltages and those expected during automotive cranking or load dump situations, while ensuring that downstream electronics are protected.

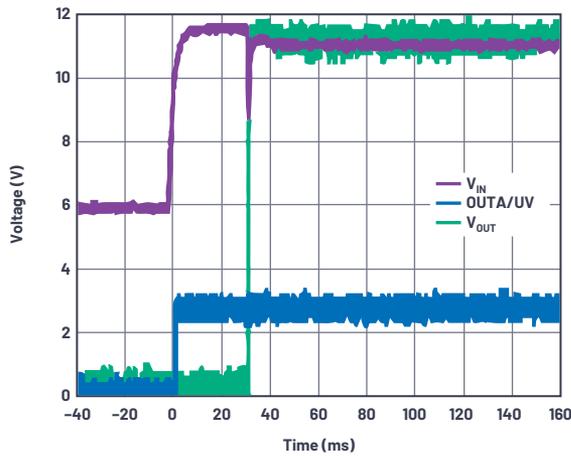


Figure 8. Expanded cranking recovery.

Figure 8 shows the cranking recovery behavior. It shows the LTC4368-2's internal recovery timer (36 ms typical) that is satisfied before the switching element is re-energized. Also observe that once the switching element is re-energized, V_{IN} is momentarily pulled low. This is due to charging the circuit's load capacitance and series input inductance. This demonstrates the need for wide voltage monitoring threshold hysteresis. This load capacitor charging transient is ignored by the LTC2966.

Load Dump Events

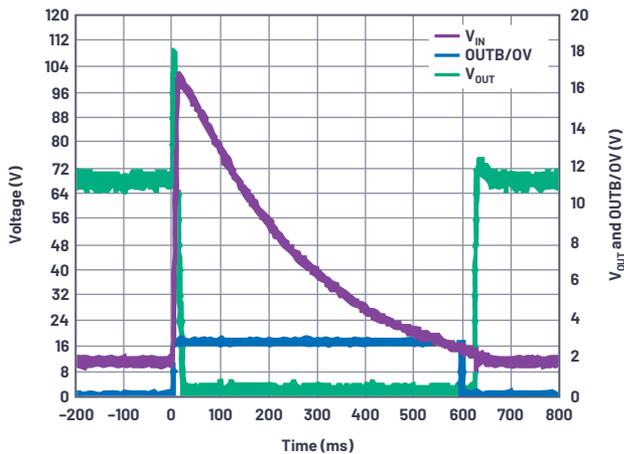


Figure 9. Complete load dump waveform.

Figure 9 shows the circuit's load dump behavior. Prior to ignition deactivation, V_{IN} is at its nominal value. The power path is active and $V_{OUT} = V_{IN}$. During the load dump event, the battery voltage pulls up to 100 V. The 18 V rising voltage monitor threshold is crossed and OUTB immediately pulls up the 0 V pin of the LTC4368-2. The LTC4368-2 responds to this by pulling its GATE pin low, which opens the power path and V_{OUT} falls to 0 V. The switching element remains open until the load dump discharges down to 15 V. Once the 15 V falling threshold is crossed, OUTB of the LTC2966 pulls down the 0 V pin of the LTC4368-2 and after the LTC4368-2 internal recovery timer expires, the LTC4368-2 energizes the switching element again.

Reverse Voltage Protection

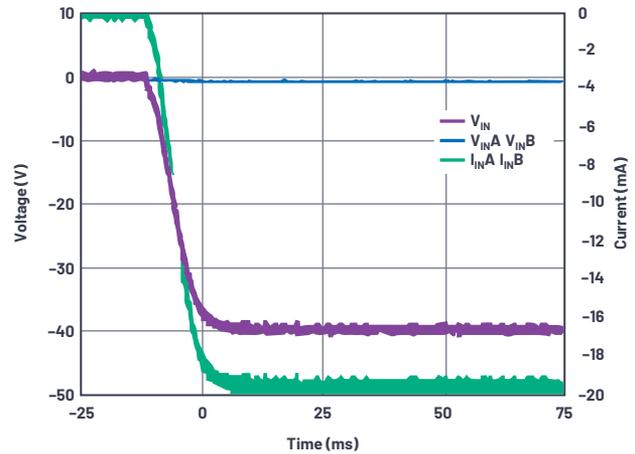


Figure 10. Reverse voltage protection measurement.

Figure 10 shows the 1.96 k Ω resistor limiting the current out of the LTC2966 supply pins during a reverse voltage event. The application's input voltage was ramped from 0 V to -40 V. The current out of the V_{INA} and V_{INB} pins is limited to 20 mA and the voltage of the V_{INA} and V_{INB} pins is held to several hundred millivolts below ground. The LTC2966 safely withstands the reverse voltage event.

Forward Overcurrent Protections

Figure 11 shows the inrush current limiting determined by R10 and C1. As expected, inrush current is limited to 1 A and V_{OUT} pulls up to 12 V cleanly without asserting the overcurrent limit.

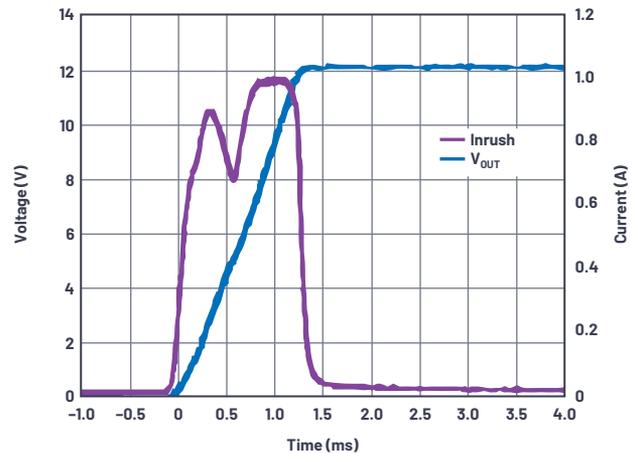


Figure 11. Inrush current limiting.

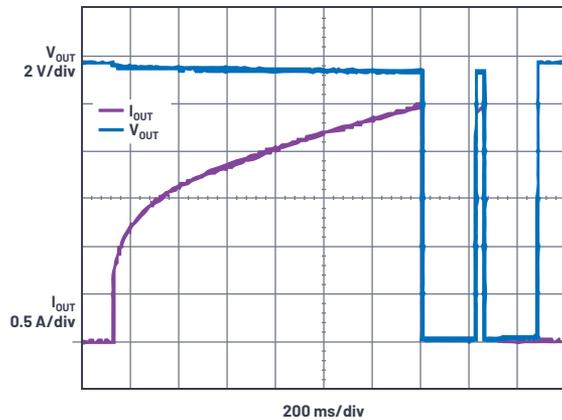


Figure 12. Assertion of forward overcurrent protection and retry delay.

Figure 12 shows the LTC4368 response to a positive overcurrent event. The positive overcurrent comparator in the LTC4368 trips when the voltage between the SENSE and V_{OUT} pins exceeds 50 mV. Current sense resistor R11 is 20 m Ω , which sets the current limit in the application to 2.5 A.

In this demonstration, the current is ramped up until the overcurrent protection asserts. As expected, the overcurrent protection activates at 2.5 A. The LTC4368 removes the load from the supply V_{OUT} and load current drops to 0 V. After the LTC4368 retry timer is satisfied, the LTC4368 reconnects the supply to the load. If the overcurrent condition is gone, then the load remains connected to the supply. Otherwise the LTC4368 removes the load from the supply. The amount of retry delay can be increased by adding capacitance to the RETRY pin. If desired, V_{OUT} can be latched off by grounding the RETRY pin. In this circuit, the retry timer is set for 250 ms. The retry timer configuration is explained in the LTC4368 data sheet.

Reverse Overcurrent Protection

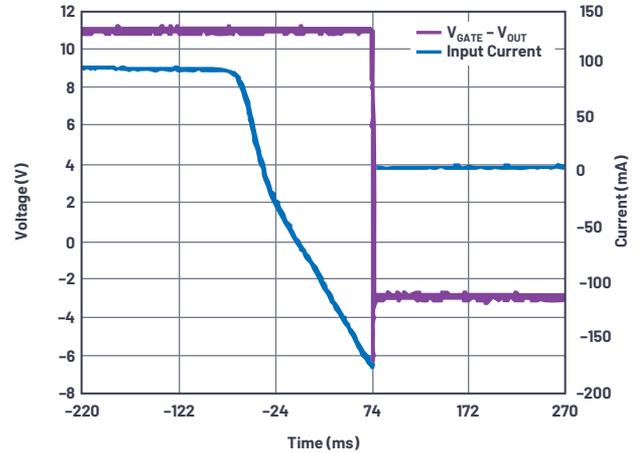


Figure 13. Assertion of reverse overcurrent protection.

Figure 13 shows the LTC4368 response to a reverse overcurrent transient. The reverse overcurrent comparator senses the voltage between the V_{OUT} and SENSE pins. The voltage threshold for reverse overcurrent assertion is version dependent. The LTC4368-1 will assert at 50 mV and the LTC4368-2 will assert at 3 mV. This application is designed with the LTC4368-2 version. Current sense resistor R11 is 20 m Ω . This sets the reverse overcurrent limit to 150 mA.

In this example, while the supply provides 100 mA to the load, a voltage step is introduced to V_{OUT} , so that V_{OUT} is larger than V_{IN} . As V_{OUT} increases, I_{LOAD} decreases. The voltage step is large enough to force current to flow from the load to the supply. This continues until the reverse current reaches 150 mA and the reverse overcurrent comparator trips. When the reverse overcurrent comparator trips, the GATE pin is pulled low. This removes the load from the supply and prevents the load from farther back driving the supply. The LTC4368 will hold the gate low until it senses V_{OUT} drop 100 mV below V_{IN} .

Conclusion

The automotive application developed in this article demonstrates that the use of specialized protection devices can simplify the implementation of automotive protection circuitry. With minimal additional circuitry, the LTC2966 and LTC4368-2 were combined to provide accurate, robust, and comprehensive transient protection. The flexibility of the devices allows them to be configured for use in numerous applications.



About the Author

Al Hinckley received his B.S.E.E. from Merrimack College, and later a Graduate Certificate in VLSI and microelectronics from UMass Lowell. He joined Linear Technology (now part of Analog Devices) in April 2005. He can be reached at albert.hinckley@analog.com.



AHEAD OF WHAT'S POSSIBLE™

For regional headquarters, sales, and distributors or to contact customer service and technical support, visit analog.com/contact.

Ask our ADI technology experts tough questions, browse FAQs, or join a conversation at the EngineerZone Online Support Community. Visit ez.analog.com.

©2020 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.

VISIT ANALOG.COM